



$$\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

A circuit diagram showing a single resistor, represented by a zigzag line, connected in series with two horizontal lines. This represents the equivalent circuit for the parallel combination of R_1 and R_2 .